

➤ Example (1)

Three identical coils, each having a resistance of $20\ \Omega$ and an inductance of $0.5\ \text{H}$ connected in (a) star and (b) delta to a three phase supply of $400\ \text{V}$; $50\ \text{Hz}$. Calculate the current and the total power absorbed by both method of connections



➤ Example (1)

Three identical coils, each having a resistance of $20\ \Omega$ and an inductance of $0.5\ \text{H}$ connected in (a) star and (b) delta to a three phase supply of $400\ \text{V}$; $50\ \text{Hz}$. Calculate the current and the total power absorbed by both method of connections

➤ First of all calculating the impedance of the coils

$$R_{\phi} = 20\Omega$$

$$X_{\phi} = 2\pi \times 50 \times 0.5 = 157\Omega$$


$$Z_{\phi} = R_{\phi} + jX_{\phi} = \sqrt{R_{\phi}^2 + X_{\phi}^2} \angle \theta \quad \text{where} \quad \theta = \tan^{-1} \left(\frac{X_{\phi}}{R_{\phi}} \right)$$

$$= \sqrt{20^2 + 157^2} \angle \tan^{-1} \left(\frac{157}{20} \right) = 158 \angle 83^{\circ}$$

$$\cos \theta = \cos 83^{\circ} = 0.1264$$



□ Y-connection

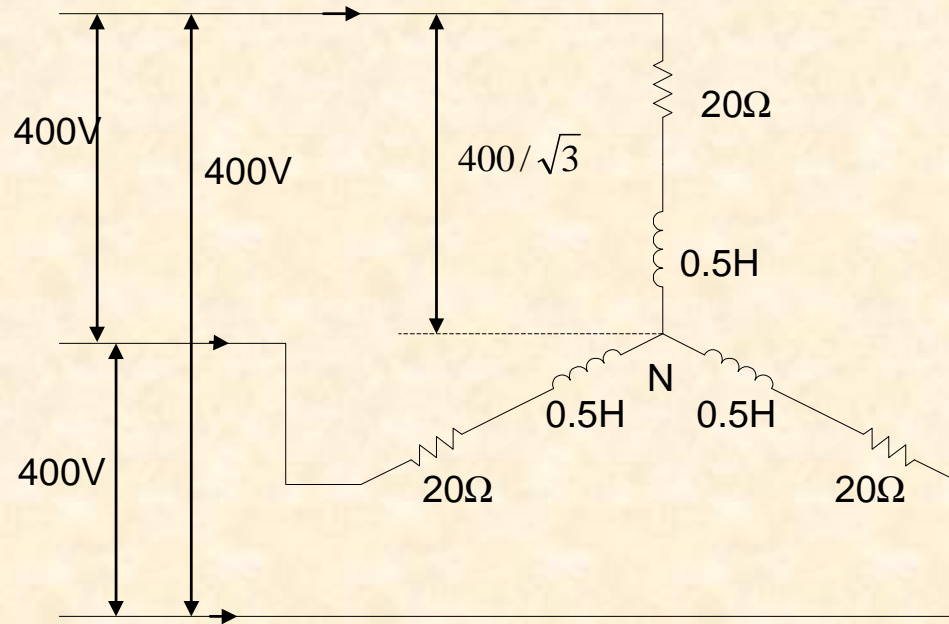

➤ Since it is a balanced load

$$V_{\phi} = \frac{400}{\sqrt{3}} = 231V \qquad I_{\phi} = I_L = \frac{V_{\phi}}{Z_{\phi}} = \frac{231}{158} = 1.46A$$

➤ Power absorbed

$$P = \sqrt{3}V_L I_L \cos \theta = \sqrt{3} \times 400 \times 1.46 \times 0.1264 = 128W$$




□ Δ-connection

$$V_{\phi} = V_L = 400V$$

$$I_{\phi} = \frac{V_{\phi}}{Z_{\phi}} = \frac{400}{158} = 2.532A$$

$$I_L = \sqrt{3}I_{\phi} = 4.385$$
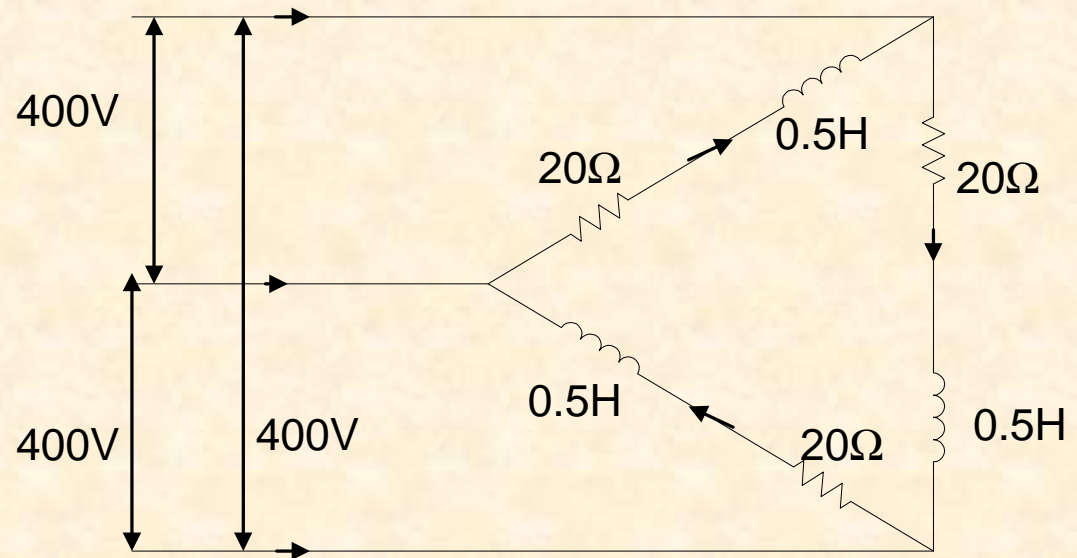
$$P = \sqrt{3}V_L I_L \cos \theta = \sqrt{3} \times 400 \times 4.38 \times 0.1264 = 384 W$$



➤ Example (2)

A balanced three-phase system with a line voltage of 300V is supplying a balanced Y-connected load with 1200W at a leading power factor (PF) of 0.8. Determine line current I_L and per-phase load impedance Z_ϕ



➤ Example (2)


A balanced three-phase system with a line voltage of 300V is supplying a balanced Y-connected load with 1200W at a leading power factor (PF) of 0.8. Determine line current I_L and per-phase load impedance Z_ϕ

The phase voltage is: $V_\phi = 300/\sqrt{3}$ V

The per-phase power is: $1200\text{W}/3 = 400$ W

Therefore $400 = \frac{300}{\sqrt{3}} (I_L) \times 0.8$, and $I_L = 2.89$ A

The phase impedance is: $|Z_\phi| = \frac{V_\phi}{I_L} = \frac{300/\sqrt{3}}{2.89} = 60\Omega$

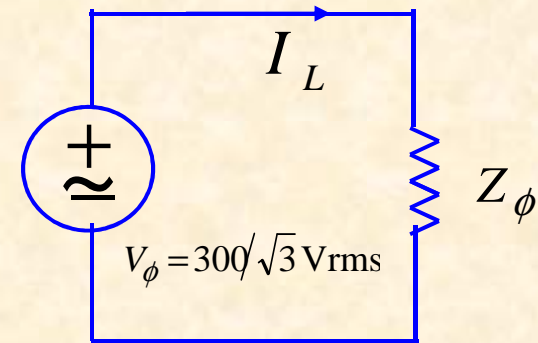

A leading PF of 0.8 implies the current leads the voltage, and the impedance angle is: $-\arccos(0.8) = -36.87^\circ$

and $Z_\phi = 60 \angle -36.87^\circ \Omega$

Note: the per-phase apparent power of a Y-Y connected load is $P = V_{an} \times I_{aA}$

(phase voltage \times line current)



➤ Example (3)

Determine the amplitude of line current in a three-phase system with a line voltage of 300V that supplies 1200W to a Δ -connected load at a lagging PF of 0.8



➤ Example (3)

Determine the amplitude of line current in a three-phase system with a line voltage of 300V that supplies 1200W to a Δ -connected load at a lagging PF of 0.8

The per-phase average power is: $1200\text{W}/3 = 400\text{W}$

Therefore, $400\text{W} = V_L \cdot I_\phi \cdot 0.8 = 300\text{V} \cdot I_\phi \cdot 0.8$, and $I_\phi = 1.667\text{A}$

The line current is : $I_L = \sqrt{3} I_\phi = \sqrt{3} \cdot 1.667\text{A} = 2.89\text{A}$

Moreover, a lagging PF implies the voltage leads the current by $\arccos(0.8) = 36.9^\circ$

The impedance is: $Z_\phi = \frac{\dot{V}_\phi}{\dot{I}_\phi} = \frac{300}{1.667} \angle 36.87^\circ = 180 \angle 36.87^\circ \Omega$

Note: the per-phase apparent power of a Δ -connected load is $P = V_{AB} \times I_{AB}$

(line voltage \times phase current)



Power System Loads

- **Single-phase power**
 - Residential and business customers
- **Single-phase and three-phase systems**
 - Industrial customers
 - Therefore, there is a need to connect both single-phase and three-phase loads to three-phase systems
- **Utility tries to connect one third of its single-phase loads to each phase**
- **Three-phase loads are generally balanced**



Power System Loads

□ Real loads

- Seldom expressed in terms of resistance, capacitance, and inductance
- Rather, real loads are described in terms of power, power factors, etc.



Measuring Power in Three-Phase Circuits

- ❑ Measuring power to a 4-wire Y load requires three wattmeters (one meter per phase)
- ✓ Loads may be balanced or unbalanced
- ✓ Total power is sum of individual powers
- ✓ If load could be guaranteed to be balanced
 - Only one meter would be required
 - Its value multiplied by 3



Measuring Power in Three-Phase Circuits

- For a three-wire system, only two meters are needed
- Loads may be Y- or Δ -connected
- Loads may be balanced or unbalanced
- Total power is algebraic sum of meter readings

